

Andy Jeong, Brenda So, Gordon Macshane

ECE 151A Spring 2016

22 February 2016


Project 1: Paper Processor

Abstract

This project aims to construct a circuit on Verilog Hardware Description Language whereby the paper processor (https://sites.google.com/site/kotukotuzimiti/Paper_Processor) is implemented. The Verilog code takes in the modules (.v) – *checking*, *dff_reset_negedge*, *dff_reset_posedge*, *halt*, *increment*, *jno*, *programcounter*, *fulladder*, *memory* – which take the inputs and outputs the data bits according to the primitive logic gates event-driven cases (always block) and time delays (#). The *instruction.bin* file takes in the instruction codes, which are picked out based on the logic, and determines the data output.

Diagram (refer to *waveform.png*)

 Waveform 1: Paper Processor implementation for time duration = 69 (ns)



Sample Output (refer to *sample_output.txt*)

VCD info: dumpfile pp.vcd opened for output.

```

time = 0    PC = xx instruct = xx out = 00 stat = 0
time = 1    PC = 00 instruct = 00 out = 00 stat = 0
time = 5    PC = 01 instruct = 01 out = 01 stat = 0
time = 13   PC = 10 instruct = 00 out = 01 stat = 0
time = 14   PC = 00 instruct = 00 out = 01 stat = 0
time = 21   PC = 01 instruct = 01 out = 01 stat = 0
time = 22   PC = 01 instruct = 01 out = 10 stat = 0
time = 29   PC = 10 instruct = 00 out = 10 stat = 0
time = 30   PC = 00 instruct = 00 out = 10 stat = 0
time = 37   PC = 01 instruct = 01 out = 10 stat = 0
time = 38   PC = 01 instruct = 01 out = 11 stat = 0
time = 45   PC = 10 instruct = 00 out = 11 stat = 0
time = 46   PC = 00 instruct = 00 out = 11 stat = 0
time = 53   PC = 01 instruct = 01 out = 11 stat = 0
time = 54   PC = 01 instruct = 01 out = 00 stat = 1
time = 61   PC = 10 instruct = 00 out = 00 stat = 1
time = 69   PC = 11 instruct = 10 out = 00 stat = 1

```

Compiling and Running the Code (refer to Makefile)***need iverilog (Icarus Verilog) and GTKwave installed**

To compile, run and show waveform using gtkwave simulator:

```
make -f Makefile
```

What is under Makefile?

```
SOURCE = main_tb.v
```

```
WAVE = gtkwave
```

```
all:
```

```
    iverilog -o pp.vvp $(SOURCE)
```

```
    vvp pp.vvp
```

```
    $(WAVE) pp.vcd
```

```
clean:
```

```
    rm -rf *.vvp *.vcd
```

Optional:

To compile separately on terminal:

```
iverilog -o <objectname> main_tb.v
```

To run the compiled object file:

```
vvp <objectname>
```

To change the instruction:

change the bits in instruct.bin

Paper Processor Design*The 2-bit Paper Processor Instructions*

inc	//increments the address, register
jno 00 ₍₂₎	//jump if not overflow
hlt	//halt
nop	//no operation

Verilog Code*Main Testbench Code (refer to main_tb.v)*

```

//
// School: The Cooper Union
// Course: ECE151A Spring 2016
// Assignment: Paper Processor
// Group members: Andy Jeong, Brenda So, Gordon Macshane
// Date: 2/22/2016
//
//-----Instructions-----
//      Instructions Guide:
//          INC: 00 (2)
//          JNO: 01 (2)
//          HLT: 10 (2)
//
//      Instructions for the 2-bit paper processor:
//          IS1:   INC
//          IS2,3: JNO 00 (2)
//          IS4:   HLT
//
`timescale 1ns/1ns

`include "memory.v"
`include "increment.v"
`include "programcounter.v"
`include "halt.v"
`include "jno.v"
`include "checking.v"
`include "dff_reset_negedge.v"
`include "dff_reset_posedge.v"

module main_tb();

    reg reg_status;                // status register
    reg reg_clock;                // clock register
    reg [1:0] reg_reset;          //used to initialize the
    program counter
    reg [1:0] reg_output;         // output
    registers

    wire wire_clock_from_jno;     //Pulse from JNO, imitating monostable timer
    wire [1:0] wire_adder_to_output; // INC logic :connect adder to reg
    out

    wire wire_adder_to_status;    // ING logic:
    ddding to status

    wire [1:0] wire_instruction_from_memory; // output
    instruction from ram

    wire [1:0] wire_instruction_checked; // actual
    instruction after checking

```

```

wire wire_monostable_clock; // monostable clock induced by inc
logic
wire wire_clock_from_halt;
    // clock induced by halt
wire wire_monostable_clock_status_0;
wire wire_enabled;
wire wire_enabled_status;
wire [1:0] wire_program_counter; // Counter:
program_counter_output

initial begin

    //print out on console
    $monitor ("PC = %b instr = %b reg = %b status = %b", wire_program_counter,
wire_instruction_from_memory, reg_output, reg_status);

    reg_clock = 0; // initialize clock to be 0
    reg_status = 0; // initialize status to be 0
    reg_output= 2'b00; // initialize value register
    reg_reset= 2'b00; // Resetting logic
    #1 reg_reset = 2'b11; //Resetting program counter
    #1 reg_reset= 2'b00;
    #80 $finish; //simulation runs for 80 seconds
end

initial begin
    $dumpfile ("pp.vcd"); //waveform file output in .vcd format
    $dumpvars;
end

always @(posedge wire_monostable_clock_status_0)
begin
    reg_output[0] <= wire_adder_to_output[0];
    reg_output[1] <= wire_adder_to_output[1];
    reg_status <= wire_adder_to_status;
end

always
    #4 reg_clock = ~reg_clock; // Generate clock

memory memory0(wire_program_counter,wire_instruction_from_memory);

programcounter pc0(wire_program_counter, wire_clock_from_jno, reg_reset,
wire_instruction_from_memory, wire_clock_from_halt, wire_enabled_status);

and a1(wire_monostable_clock_status_0, wire_monostable_clock, !reg_status);

checking checking0(wire_instruction_checked, wire_enabled,
wire_instruction_from_memory);

```

```

increment increment0(wire_adder_to_output,
wire_adder_to_status,wire_monostable_clock,wire_clock_from_halt,
reg_output,wire_instruction_checked);

jno jno0(wire_enabled, wire_enabled_status, wire_clock_from_jno, reg_status,
wire_instruction_checked, wire_clock_from_halt);

halt halt0(wire_clock_from_halt, reg_clock,
wire_instruction_checked);

endmodule

```

checking.v

```

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Module Name: checking.v
// Description: checks if either of two inputs is HIGH at a certain time
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

`timescale 1ns / 1ns

module checking(instruct_checked, enabled, instruct_from_jno);

//-----Input Ports-----
input [1:0] instruct_from_jno;
input enabled;

//-----Output Ports-----
output [1:0] instruct_checked;

//input and output can be declared again as wires to pass into modules
wire [1:0] instruct;
wire enabled;
wire [1:0] instruct_checked;

or o1(instruct_checked[1], enabled, instruct_from_jno[1]);
or o2(instruct_checked[0], enabled, instruct_from_jno[0]);

endmodule

```

dff_reset_negedge.v

```
//////////////////////////////////////////////////////////////////
// Module Name: dff_reset_negedge.v
// Description: D flip flop that sets and resets at negedge
//////////////////////////////////////////////////////////////////

`timescale 1ns / 1ns

module dff_reset_negedge (clk, s, r, d, output_q, output_not_q);
    input clk, s, r, d;
    output output_q, output_not_q;
    reg output_q, output_not_q;
    always @(negedge r) begin
        output_q = 1'b0;
        output_not_q = 1'b1;
    end

    always @(negedge s) begin
        output_q = 1'b1;
        output_not_q = 1'b0;
    end

    always @(posedge clk) begin
        output_q = d;
        output_not_q = ~d;
    end

endmodule
```


dff_reset_posedge.v

```
//////////////////////////////////////////////////////////////////  
// Module Name: dff_reset_posedge.v  
// Description: D flip flop that sets and resets at posedge  
//////////////////////////////////////////////////////////////////  
  
`timescale 1ns / 1ns  
  
module dff_reset_posedge (clk, s, r, d, output_q, output_not_q);  
    input clk, s, r, d;  
    output output_q, output_not_q;  
    reg output_q, output_not_q;  
    always @(posedge r) begin  
        output_q = 1'b0;  
        output_not_q = 1'b1;  
    end  
  
    always @(posedge s) begin  
        output_q = 1'b1;  
        output_not_q = 1'b0;  
    end  
  
    always @(posedge clk) begin  
        output_q = d;  
        output_not_q = ~d;  
    end  
  
endmodule
```

halt.v

```

////////////////////////////////////
// Module Name: halt.v
// Description: takes clock input and according to the current instruction it
// determines if the clock should go on or not
////////////////////////////////////

`timescale 1ns / 1ns

module halt(pulse, clk, instruction_from_jno);

//-----Input Ports-----
input [1:0] instruction_from_jno;    //input a 2 bit register from JNO
input clk;

//-----Output Ports-----
output pulse;

wire [1:0] instruct;
wire clk;
wire pulses;
wire [1:0] w;

//-----Instructions-----

and a1(w[1], instruction_from_jno[1], !instruction_from_jno[0]);
not n1(w[0], w[1]);
and(pulse, clk, w[0]);

endmodule

```

increment.v

```

/////////////////////////////////////////////////////////////////
// Module Name: increment.v
// Description: increments 2-bit value from previous
/////////////////////////////////////////////////////////////////

`timescale 1ns / 1ns

`include "fulladder.v"

module increment(adder_to_output, adder_to_status, output_monostable, output_pulse,
out, instruct_checked);

//-----Input Ports-----
input [1:0] instruct_checked;    //input a 2 bit register from JNO
input [1:0] out;
input output_pulse;

//-----Output Ports-----
inout [1:0] adder_to_output;
output adder_to_status;
output output_monostable;

//input and output can be declared again as wires to pass into modules
wire [1:0] instructA;
wire [1:0] out;
wire output_pulse;
wire [1:0] adder_to_output;
wire status;
reg output_monostable;

//-----Intermediate Wires-----
wire w1;

//-----instructions-----

and (w1, output_pulse, !instruct_checked[1], !instruct_checked[0]);

initial begin
output_monostable = 0;
end

always @(posedge w1)
begin
    output_monostable = 1;
    #2
    output_monostable = 0;
end

```

```

fulladder adder(adder_to_status, adder_to_output, out);

endmodule

```

jno.v

```

/////////////////////////////////////////////////////////////////
// Module Name: jno.v
// Description: from the current instructions, outputs ENABLE for checking and counter
/////////////////////////////////////////////////////////////////
`timescale 1ns/1ns

module jno(enable, enable_status, openpulse, sta, instruct, pulses);

//-----Input Ports-----

input [1:0] instruct;    //input a 2 bit register from JNO
input pulses;
input sta;

//-----Output Ports-----

output enable;
output enable_status;
output openpulse;

//-----Input ports Data Type-----
// By rule all the input ports should be wires
wire [1:0] instruct;
wire pulses;
wire sta;

//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
wire enable;
wire enable_status;

//-----Intermediate Wires-----
reg s;
reg r;
wire not_enable, not_enable_status;
wire w1, w2;
reg mem;
reg pulser;
wire openpulse;
reg openpulser;

//-----Instructions-----

```

```
initial begin
s = 0;
r = 0;
pulser = 0;
openpulser = 0;
end

and a1(w1, !instruct[1], instruct[0]);
and a2(w2, !sta, !instruct[1], instruct[0]);
and a3 (openpulse, !sta, openpulser);

always @(posedge w1)
begin
    #1
    pulser = 1;
    #8
    openpulser = 1;
    #4
    openpulser = 0;
    #1
    pulser = 0;
    #1
    pulser = 1;
    #1
    pulser = 0;
end
dff_reset_negedge dff3(pulser, s, r, w1, enable, not_enable); //enabling the checking
dff_reset_negedge dff4(pulser, s, r, w2, enable_status, not_enable_status); //enabling
for counter

endmodule
```

programcounter.v

```

////////////////////////////////////
// Module Name: programcounter.v
// Description: counter
////////////////////////////////////

`timescale 1ns / 1ns

module programcounter(select, clk_pulse, reset, input_from_jno, clk, enabled);

//-----Input Ports-----

input [1:0] input_from_jno;    //input a 2 bit register from JNO
input clk;                    //input clock signal
input enabled;                //input enabling JNO register addresses
input [1:0] reset;           //for resetting
input clk_pulse;

//-----Output Ports-----

output [1:0] select;

//-----Input ports Data Type-----
// By rule all the input ports should be wires
wire [1:0] input_from_jno;
wire clk;
wire enabled;
wire [1:0] R;
wire clk_pulse;

//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
wire [1:0] select;

//-----Intermediate Wires-----

wire [1:0] wire_select_from_logic;
wire w1, w2,w3,w4, w5, w6;
wire [1:0] wire_d_ff_input;
wire [1:0] wire_set_from_logic;
wire [1:0] wire_reset_from_logic;

//-----Instructions-----
and a1(wire_set_from_logic[0], clk_pulse, enabled, input_from_jno[0]);
and a2(wire_set_from_logic[1], clk_pulse, enabled, input_from_jno[1]);
and a3(w3, clk_pulse, enabled, !input_from_jno[0]);
and a4(w4, clk_pulse, enabled, !input_from_jno[1]);
or o1(wire_reset_from_logic[0], w3, reset[0]); //R[0] is 0, w1 goes from 0 to 1
or o2(wire_reset_from_logic[1], w4, reset[1]); //

```

```

dff_reset_posedge dff0(clk, wire_set_from_logic[0], wire_reset_from_logic[0],
wire_d_ff_input[0], select[0], wire_select_from_logic[0]);
dff_reset_posedge dff1(clk, wire_set_from_logic[1], wire_reset_from_logic[1],
wire_d_ff_input[1], select[1], wire_select_from_logic[1]);

and a5(w1, wire_select_from_logic[0], select[1]);
and a6(w2, wire_select_from_logic[1], select[0]);
or o3(wire_d_ff_input[1], w1, w2);
and a7(wire_d_ff_input[0], wire_select_from_logic[0],1);

endmodule

```

fulladder.v

```

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Module Name: fulladder.v
// Description: Full Adder where 1 is always added to the previous number
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

`timescale 1ns / 1ns

module fulladder(status, sum, a);

//-----Input Ports-----

inout [1:0] a; //input a 2 bit register

//-----Output Ports-----

output [1:0] sum; //output 2 bit registers
output status; //see whether registers overflown

//-----Input ports Data Type-----
// By rule all the input ports should be wires
wire [1:0] a;
wire [1:0] b;

//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
wire [1:0] sum;
wire status;

//-----Intermediate Wires-----
wire w0, w1, w2, w3;

//-----Instructions-----

```

```

//set LSB of input to sum[0]
xor u0(sum[0],a[0], 1'b1);

//set MSB of input to sum[1]
and u1(w0, a[0], 1'b1);
xor u2(w1, a[1], 1'b0);
and u3(w2, a[1], 1'b0);
and u4(w3, w0, w1);
xor u5(sum[1], w0, w1);

//set carry out to be status
or u6(status,w2, w3);

endmodule

```

memory.v

```

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Module Name: memory.v
// Description: loads data from instruction binary file
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

`timescale 1ns / 1ns

module memory(addr, data);

parameter Instructions = "./instruction.bin";

//-----Input Ports-----
input [1:0] addr;

//-----Output Ports-----
output [1:0] data;

reg [1:0] ram_reg [0:3];
wire [1:0] addr;
wire [1:0] data;

//-----load instructions-----
//2 bit wide, 4 bit deep register memory
initial begin
    $readmemb(Instructions, ram_reg);
end

assign data = ram_reg[addr];

endmodule

```